

100rtdaysChallenge

#DAY16

DATE: 14/10//2023

AIM:

TO DESIGN A 100 BIT BINARY ADDER THAT ADDS TWO 100 BIT NUMBERS AND A CARRY_IN TO PRODUCE A 100 BIT SUM AND A CARRY OUT.

DESIGN CODE:

```
//defining full adder module
module full_adder(

input  x              ,
input  y              ,
input  carry_in       ,
output sum            ,
output carry_out
)

assign    sum=x^y^carry_in                ; //sum
assign    carry_out=x&y |y&carry_in |carry_in&x ; //carry
endmodule


//defining top module 100 bit adder
module _100_bit_adder(
    input  [99:0] p,
    input  [99:0] q,
    input  c_in,
    output [99:0] s,
    output  c_out
);
```

```

    wire [99:0] carry;
        //assigning values to first full adder
    full_adder
    FA(.x(p[0]),.y(q[0]),.carry_in(c_in),.sum(s[0]),.carry_out(car
ry[0]));
    genvar i;
        //for loop for rest of the 99 full adders
    generate
        for (i=1;i<100;i=i+1) begin

            full_adder FA(.x(p[i]),.y(q[i]),.carry_in(carry[i-
1]),.sum(s[i]),.carry_out(carry[i]));

        end
    endgenerate

    assign c_out=carry[99];

endmodule

```

SIMULATION:

